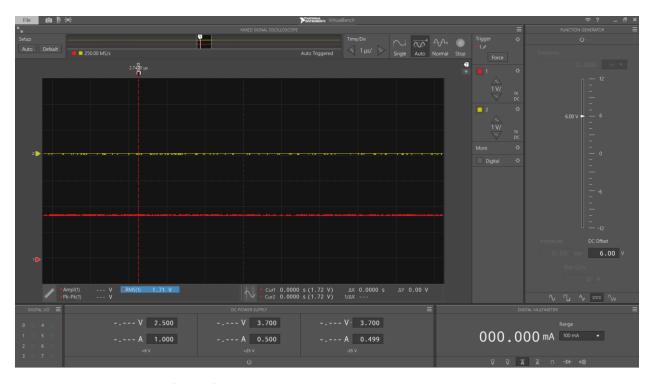



No diode, no cap - FLYBACK (239 mV - 1.67 V)




Diode, no cap -- FLYBACK (1.72 V)




Cap, no diode – FLYBACK

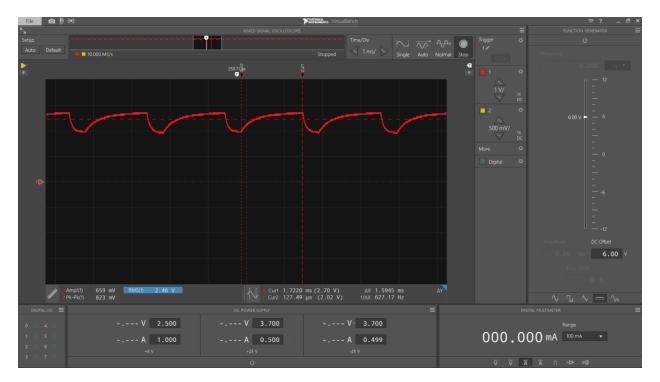

Cap, no diode – VCC (2.02 V - 2.70 V)

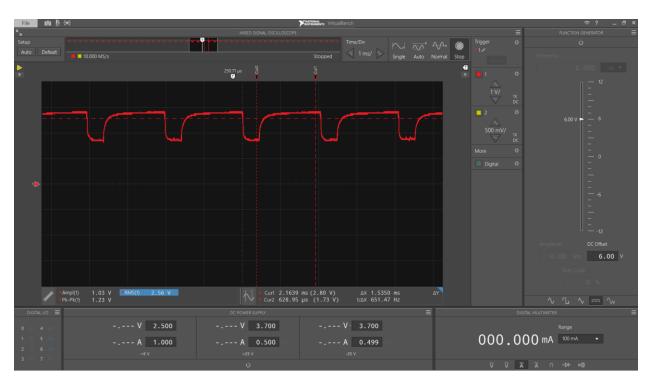


No cap, no diode – VCC (1.73 V – 2.80 V)

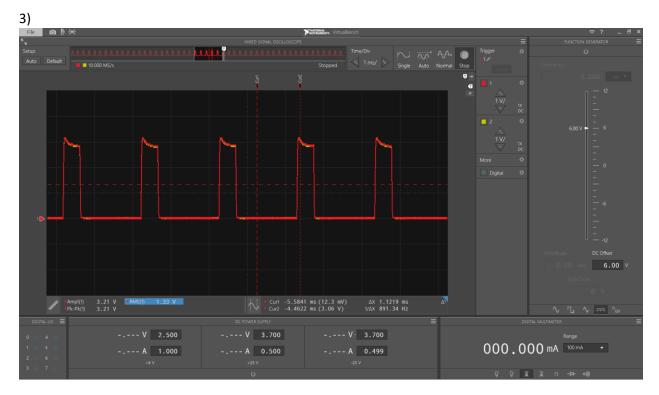

Channel 1 – PWM, Channel 2 – Filtered (~0 – ~3 V for both)

--No difference, no effect

4)

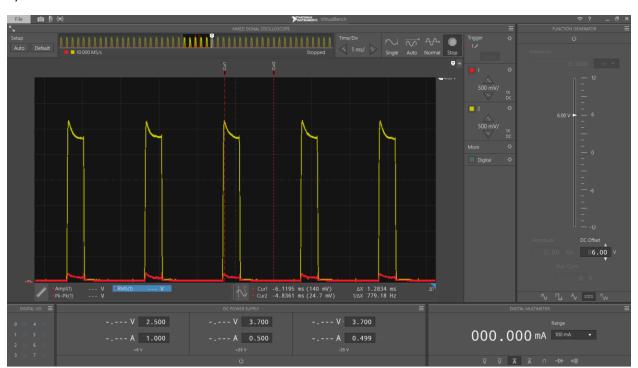

Channel 1 – Flyback (140 MV), Channel 2 – Filtered (Difference of \sim 3.2 V)